

#### **ABSTRACT**

This application note will highlight characteristics of Pletronics Low Voltage Differential Signal (LVDS) frequency control products and provide guidance for proper termination.

This signal type or logic type is significantly different than TTL or CMOS logic and does require special consideration to utilize the logic properly.

The terms ECL, PECL and LVPECL are reviewed.

The Application Note covers interfacing LVDS to other logic types:

- LVDS to CML
- LVDS to HSTL
- LVDS to LVDS

The importance of this logic is that it provides:

- Very high frequency operation
- Minimal EMI/RFI due to differential clock signals
- The low impedance differential outputs provide many implementation options.

The application of the Pletronics LV77, LV88 and LV99 LVDS families is reviewed.



### **TABLE OF CONTENTS**

1 Introduction: Pletronics LVDS Output Oscillators	
1.1 History of LVDS	3
1.2 About LVDS Drivers	
1.3 What differentiates the Pletronics LV7, LV8 and LV9 series clock oscillators?	4
2 Interfacing LVDS Outputs to Other Logic Inputs	
2.1 Interface LVDS to LVDS with Termination On the PCB	5
2.2 Interface LVDS to LVDS with Termination Internal in the Destination IC	5
2.3 Interface LVDS to LVDS with Termination Split and a Capacitor	6
2.4 Interface LVDS to CML	6
2.5 Interface LVDS to HSTL	7
2.6 Example of Driving 2LVDS inputs with no clock skew	8
IMPORTANT NOTICE	9



#### 1 INTRODUCTION: PLETRONICS LVDS OUTPUT OSCILLATORS

Hooray for standardization. Unlike its cousins from other logic families, LVDS is standardized. Standards bodies define LVDS in specification ANSI/TIA/EIA-644A. Logic families such as Low-Voltage Positive Emitter Coupled Logic (LVPECL) and Current-Mode Logic (CML) are widely used but neither technology has been standardized by any official standards organization. Implementation of these logic families is vendor specific so a careful specification review is important.

#### 1.1 HISTORY OF LVDS

National Semiconductor first introduced LVDS as a standard in 1994. National recognized that the demand for bandwidth was increasing at an exponential rate while users also desired low power dissipation. The demands exceeded the speed capabilities of RS-422 and RS-485 differential transmission standards. While Emitter Coupled Logic (ECL or PECL) was available at the time, it can be difficult to interface with standard logic levels.

Output	LVDS	PECL 3.3V	PECL 2.5V	
V <sub>OH</sub> (Minimum)	1.249 V	2.27 V	1.47 V	
V <sub>OL</sub> (Maximum)	1.252 V	1.68 V	0.88 V	

The LVDS levels do not change with supply voltage.

The PECL output levels follow the supply voltage. The values shown are for the nominal supply voltage only.

Input	t LVDS PECL PECL 3.3V 2.5V		HSTL	CML	
V <sub>REF</sub> or V <sub>CM</sub>	1.20 V	2.00 V	1.20 V	0.75 V	V <sub>CC</sub> - 0.40 V
V <sub>ID</sub> (Minimum)	200 mV	310 mV	310 mV	400 mV	400 mV
V <sub>IH</sub> (Minimum)	finimum) 1.249 V		1.47 V	V <sub>REF</sub> + 0.2 V	V <sub>cc</sub>
V <sub>IL</sub> (Maximum)	1.252 V	1.68 V	0.88 V	V <sub>REF</sub> - 0.2 V	V <sub>CC</sub> - 0.40 V


#### Some of the advantages of LVDS are:


- Lower power than other technologies
- Output signal that is power supply independent
- Low voltage power supply compatibility
- Low generation of noise (EMI/RFI)
- High noise rejection
- Reliable signal distribution
- Ability to drive longer line lengths than CMOS


 
#### 1.2 ABOUT LVDS DRIVERS

The LVDS output is essentially "H Bridge" type driver. This can be realized with MOS or BJT devices.



 

The termination is 100 ohms connected between the Out and Out\*. The InX nodes are driven from the internal circuitry. The output states are:

Output	Q1	Q2	Q3	Q4	Out	Out*	Output
Logic 1	Off	On	On	Off	+3.5 mA	-3.5 mA	+350 mV
Logic 0	On	Off	Off	On	-3.5 mA	+3.5 mA	-350 mV

#### 1.3 What differentiates the Pletronics LV7, LV8 and LV9 series clock oscillators?

Pletronics provides an assortment of LVDS output solutions. These solutions all meet the ANSI/TIA/EIA-644 LVDS specification, but differ in the method of achieving the output frequency. The VPU7 VCXO family has the same characteristics as LV9.

Characteristics	LV7	LV8	LV9
Crystal Mode Used 3 <sup>rd</sup> Overtone		Fundamental	Fundamental
Frequency Range	quency Range 80 to 325MHz		10.9MHz to 700MHz
Supply Voltage	1.8V, 2.5V and 3.3V	3.3V	3.3V
Multiplication Method	none	Low Noise PLL with an LC VCO phase locked to the crystal	Low Noise PLL with an LC VCO phase locked to the crystal
Process Technology BiCMOS		RF SiGe BiCMOS	RF SiGe BiCMOS
Phase Noise	excellent		
Jitter			Good
Tr and Tf	Good	Good	Excellent (very fast)



#### 2 INTERFACING LVDS OUTPUTS TO OTHER LOGIC INPUTS

From time to time, it may be necessary to support other logic families. Pletronics supplies a wide assortment of CMOS and LVPECL oscillators. For those applications, it is only necessary to select the correct device. Basic termination of LVDS is covered along with examples of how to terminate to other logic types.


Pletronics provides specification compliant LVDS products in 5x7mm (LV77 series) and 3.2x5mm (LV55 series) Crystal Oscillators (XO) and 5x7mm Voltage Controlled Crystal Oscillators (VCXO) (VLU7 series). Frequencies are available from 1MHz to 670MHz in commercial (-10 to +70oC) or industrial (-40 to +85oC) temperature ranges. Pletronics manufactures LVDS devices with supply voltages of 3.3v, 2.5v and 1.8v.

Termination of specification compliant LVDS devices is simple. The termination network is a single 100-Ohm resistor across the receiver input. Unlike LVPECL, LVDS receivers have a wide common mode range so they are effectively power supply agnostic. Devices with power supply voltages of 3.3v, 2.5v and 1.8v interoperate without the need for special termination gymnastics or AC coupling.

AC coupling options are shown but one must then remember there is a low frequency limit that must be observed. The low frequency limit is set by the capacitor values and associates resistors.

 
#### 2.1 INTERFACE LVDS TO LVDS WITH TERMINATION ON THE PCB

A single 100 ohm terminating resistor placed at the end of the signal path is all that is needed. The end of the path is after the pads to the destination LVDS inputs.


 
#### 2.2 INTERFACE LVDS TO LVDS WITH TERMINATION INTERNAL IN THE DESTINATION IC


This is the simplest of all configurations and with the termination internal to the receiving device results in the best signal integrity. Many of the FPGAs permit this option to be





 
#### 2.3 INTERFACE LVDS TO LVDS WITH TERMINATION SPLIT AND A CAPACITOR

The designer could split the 100 ohm termination resistor into two 50 ohm resistors, resulting in a node in the middle of the termination that, if all is balanced, is 1.2V DC. To terminate any unbalanced noise within the differential transmission line as well as correct for any line length mismatches, a capacitor (C1) can be placed from this balanced node to ground. A recommended value is 0.01uF made with X7R dielectric.


 
#### 2.4 INTERFACE LVDS TO CML

Pletronics does not supply CML specific devices. Instead, it is possible to connect an LVDS oscillator directly to CML logic. Since CML inputs incorporate termination resistors and in many cases the bias voltage the only external components required are the two coupling capacitors (CA) and optionally two resistors (RA) to set VCM if the internal bias is not set. This example does assume the CML internal termination is 50 ohms.




Condition	RA (ohms)	
Internal V <sub>CM</sub> bias	None	
V <sub>CC</sub> = 5.0V	1200	
V <sub>CC</sub> = 3.3V	775	
V <sub>CC</sub> = 2.5V	575	
V <sub>CC</sub> = 1.8V	400	



As mentioned earlier, CML is not standardized so vendor-to-vendor differences may and do exist. If the CML receiver lacks one or both of these, an external resistor network will be required. Consult the receiver's data sheet for recommendations.
 
#### 2.5 INTERFACE LVDS TO HSTL

The interface to HSTL is more complicated for the DC connection case. This requires matching the impedances, level shifting the LVDS signal while maintaining the proper bias levels on the LVDS driver.



The resistor values must meet these criteria

$$\frac{V_{CM}}{V_{CC}} = \frac{RB + RC}{RA + RB + RC}$$
$$\frac{V_{REF}}{V_{CC}} = \frac{RC}{RA + RB + RC}$$

$$V_{CM} = 1.2$$
 for LVDS

$$V_{REF} = 0.75$$
 for HSTL

Solving the equations results in these values.

V <sub>CC</sub> (V)	RA (ohms)	RB (ohms)	RC (ohms)
3.3 140		30	50
2.5	100	36	60




#### 2.6 Example of Driving 2 LVDS inputs with no clock skew

The LVDS output is flexible and variations can be used. The requirement and conditions are:

- LVDS clock needed to drive two LVDS devices
- The LVDS receivers permitted external terminating resistors
- The should be no clock skew between the two receivers
- Adding an LVDS buffer and the resulting jitter addition was a concern
- Board space and power was at a premium

The minimum level of the LVDS receivers is such that a somewhat attenuated signal will work properly. There is no reason that 50 ohm loads are needed on the transmission lines. In this case 75 ohm terminations were chosen. This results in the LVDS signal being attenuated by 25%.

 The LVDS clock was placed between the two LVDS receivers, the 150 ohm termination resistors were placed at the end of each path. Then making the 'Electrical Path L1' the exact same as 'Electrical Path L2' solved the required clock skewing be zero.





#### **IMPORTANT NOTICE**

Pletronics Incorporated (PLE) reserves the right to make corrections, improvements, modifications and other changes to this product at any time. PLE reserves the right to discontinue any product or service without notice. Customers are responsible for obtaining the latest relevant information before placing orders and should verify that such information is current and complete. All products are sold subject to PLE's terms and conditions of sale supplied at the time of order acknowledgment.

PLE warrants performance of this product to the specifications applicable at the time of sale in accordance with PLE's limited warranty. Testing and other quality control techniques are used to the extent PLE deems necessary to support this warranty. Except where mandated by specific contractual documents, testing of all parameters of each product is not necessarily performed.

PLE assumes no liability for application assistance or customer product design. Customers are responsible for their products and applications using PLE components. To minimize the risks associated with the customer products and applications, customers should provide adequate design and operating safeguards.

PLE products are not designed, intended, authorized or warranted to be suitable for use in life support applications, devices or systems or other critical applications that may involve potential risks of death, personal injury or severe property or environmental damage. Inclusion of PLE products in such applications is understood to be fully at the risk of the customer. Use of PLE products in such applications requires the written approval of an appropriate PLE officer. Questions concerning potential risk applications should be directed to PLE.

PLE does not warrant or represent that any license, either express or implied, is granted under any PLE patent right, copyright, artwork or other intellectual property right relating to any combination, machine or process which PLE product or services are used. Information published by PLE regarding third-party products or services does not constitute a license from PLE to use such products or services or a warranty or endorsement thereof. Use of such information may require a license from a third party under the patents or other intellectual property of the third party, or a license from PLE under the patents or other intellectual property of PLE.

Reproduction of information in PLE data sheets or web site is permissible only if the reproduction is without alteration and is accompanied by associated warranties, conditions, limitations and notices. Reproduction of this information with alteration is an unfair and deceptive business practice. PLE is not responsible or liable for such altered documents.

Resale of PLE products or services with statements different from or beyond the parameters stated by PLE for that product or service voids all express and implied warranties for the associated PLE product or service and is an unfair or deceptive business practice. PLE is not responsible for any such statements.

**Contacting Pletronics Inc.** 

Pletronics Inc. 19013 36th Ave. West Lynnwood, WA 98036-5761 USA Tel: 425-776-1880 Fax: 425-776-2760

E-mail: ple-sales@pletronics.com

URL: www.pletronics.com

Copyright © 2009 Pletronics Inc.